


Overview GSI TDC-Systems

Henning Heggen
Helmholtz DTS Workshop 2017
2017 October 16-17 at KIT

TDC Concepts

ASIC

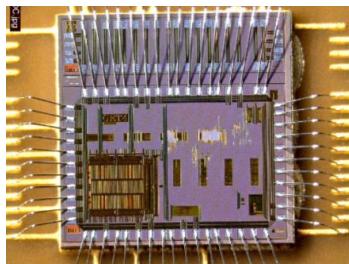- Radiation tolerance
- Low power
- Small solution size
- Fast / low dead time



FPGA TDC

- Flexibility
- Tailored to needs
- Off-the-shelf components
(availability)




No clear winner

Matter of taste / particular needs

FPGA TDC - Architecture

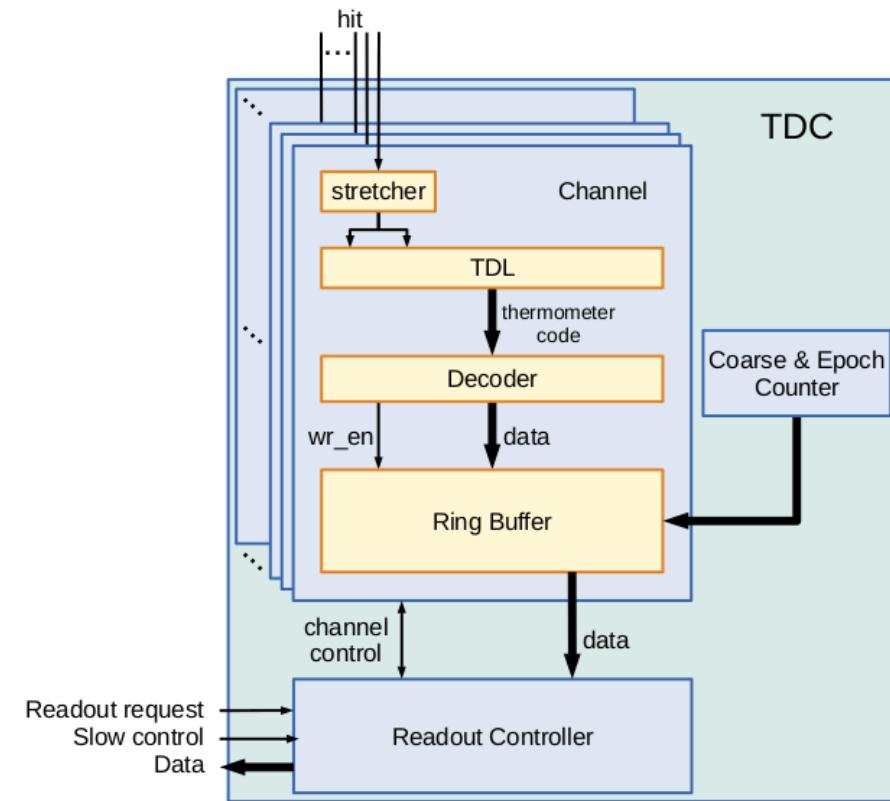
- Edge-to-pulse input stage (stretcher)
- Tapped Delay Line (TDL) as fine time interpolator
- Decoder for time information: thermometer code → binary
- Run-time counter (coarse and epoch counter) for continuous measurement range
- Ring buffer for hit history in triggered readout




Schematic view of the TDC architecture [1]

Tapped Delay Line

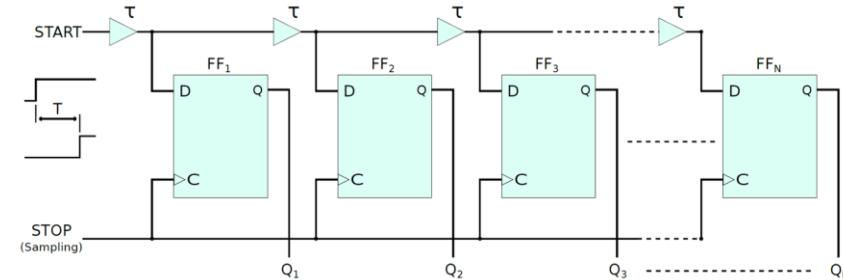
- Look-up table (LUT) and carry chain as delay element
 - Shortest delay element (bin) in FPGA
 - Placed manually
- Start signal (pulse edge) propagates along delay line and is latched at every LUT
- Propagation is stopped by common stop signal
 - 200 MHz clock for min. skew
- Time information composed out of fine time from delay line and run-time counter values



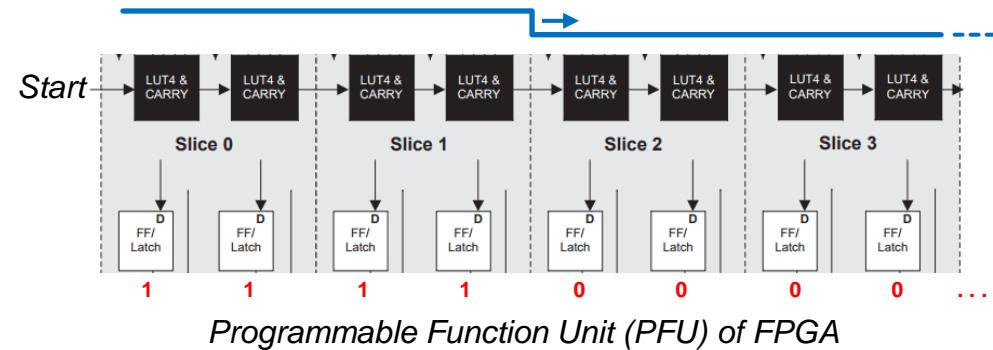Tapped Delay Line method with common stop signal [1]



Programmable Function Unit (PFU) of FPGA

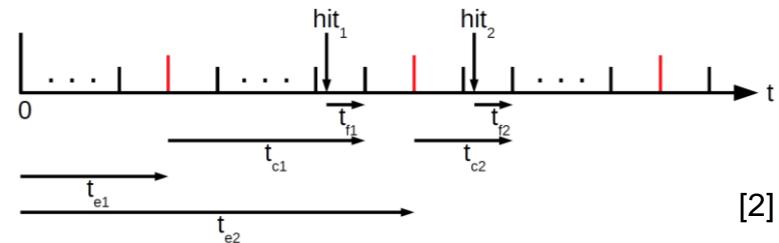



$$\Delta t = (t_{e2} + t_{c2} - t_{f2}) - (t_{e1} + t_{c1} - t_{f1})$$

Bin Widths / Non-Linearity

- Delay elements (bins) very non-uniform
 - Avg. bin width: 20 ps
 - Max. bin width: 50 ps
- Improvement through Wave Union Launcher [3]:
 - Send multiple transitions to delay line per hit signal
 - Trade-off: Precision vs. number of CH / dead time
- For two transitions
 - Avg. bin width: 10ps
 - Max. bin width: 35 ps
 - But non-linearity even worse



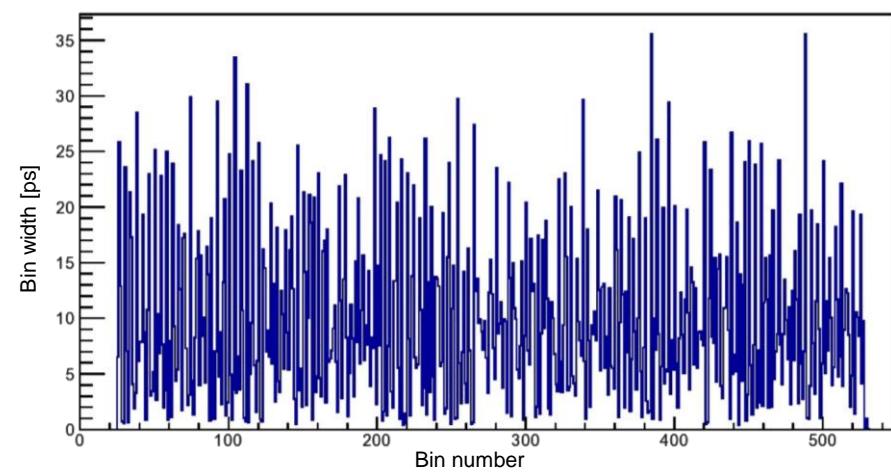
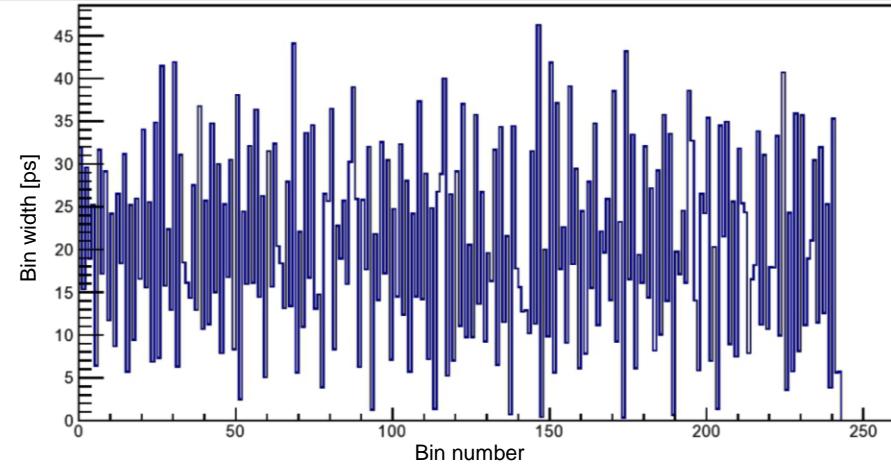
Wave union TDC: One hit, two (or more) transitions



$$\text{Bin width}_n = T_{\text{clock}} * N_{\text{bin}} / N_{\text{tot}}$$


FPGA TDC Performance

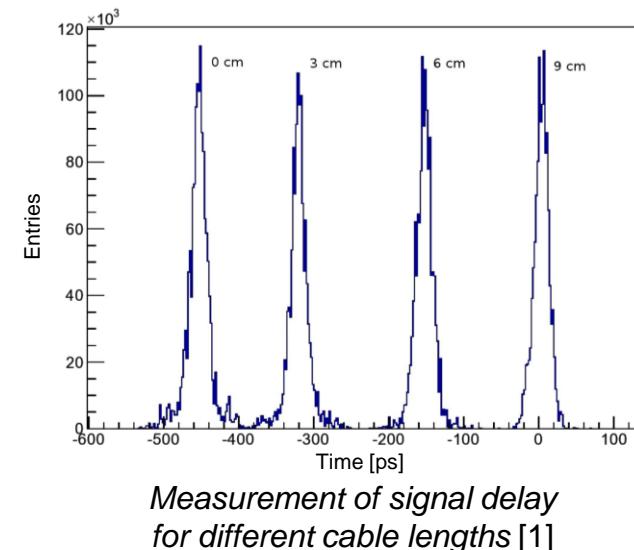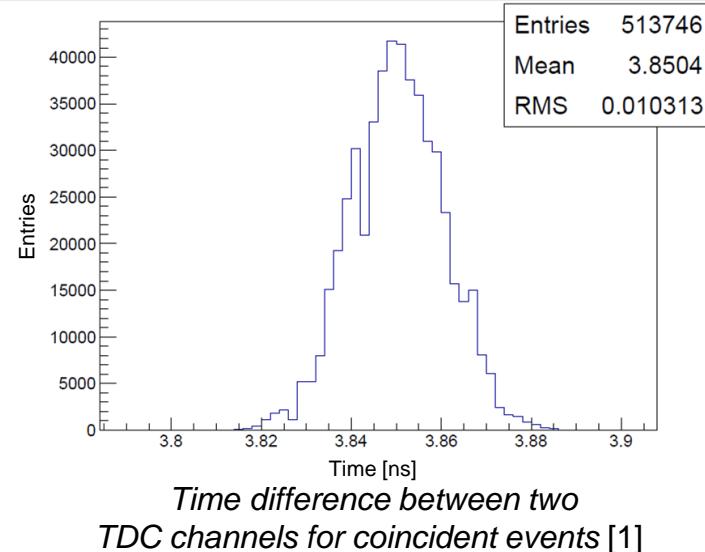- Precision (calibrated): 10 ps (between two channels w/o fitting or cuts of the data)
- Min. pulse width: 500 ps (for 100% efficiency)
- Dead time: $T_d = 30$ ns
- Up to 64 CH per FPGA (Lattice ECP3 150k)
- TDC can be configured for time-difference (ToF) or pulse width / time over threshold (ToT) measurements




FPGA TDC Calibration

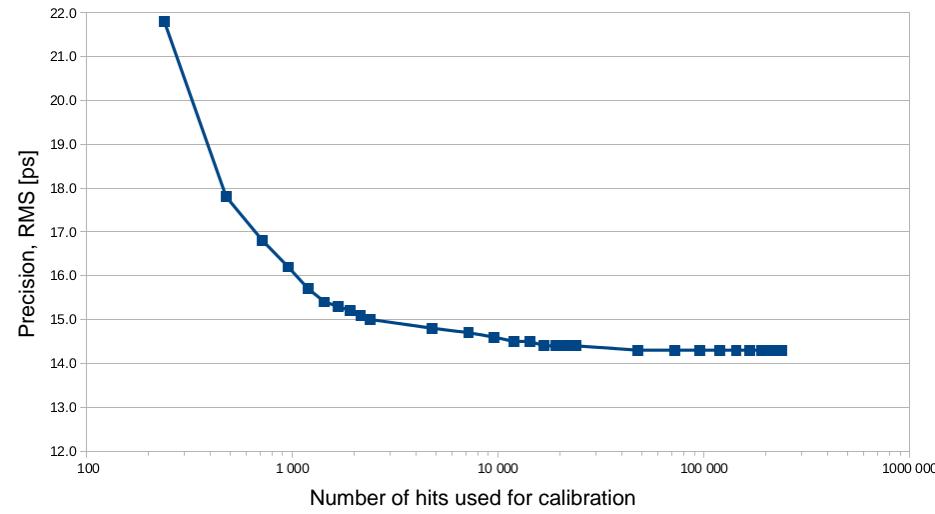- Due to intrinsic non-linearity of delay line, calibration is necessary for best results
- Look-up table with bin widths calculated from set of random hits (“box diagram”)
 - $BW_n = T_{clock} * N_{bin} / N_{tot}$
- Delay line (bin widths) temperature dependent
- Calibration needs to be updated with temperature changes



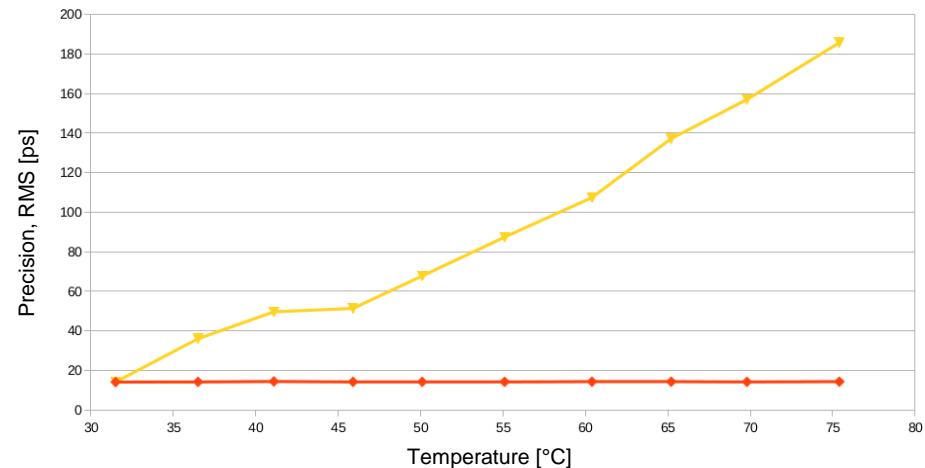Precision vs. number of hits used for calibration [2]



Temperature dependence of precision with & w/o recalibration [2]

TDC Hardware – TRB Platform





- Platform for TDC measurements incl. data readout & analysis tools
- Central FPGA as trigger system & GbE controller
- 4 peripheral FPGAs with up to 256 TDC channels total
- Flexible with many add-ons & front-ends
 - Hubs to connect multiple TRBs
 - NIM/ECL input
 - ADC
 - Standard 100mil pins (LVDS in)
 - Adapters for various front-ends (FEEs)

TDC Hardware – Front-Ends

PADIWA

Pre-amplifying & discriminating FEE

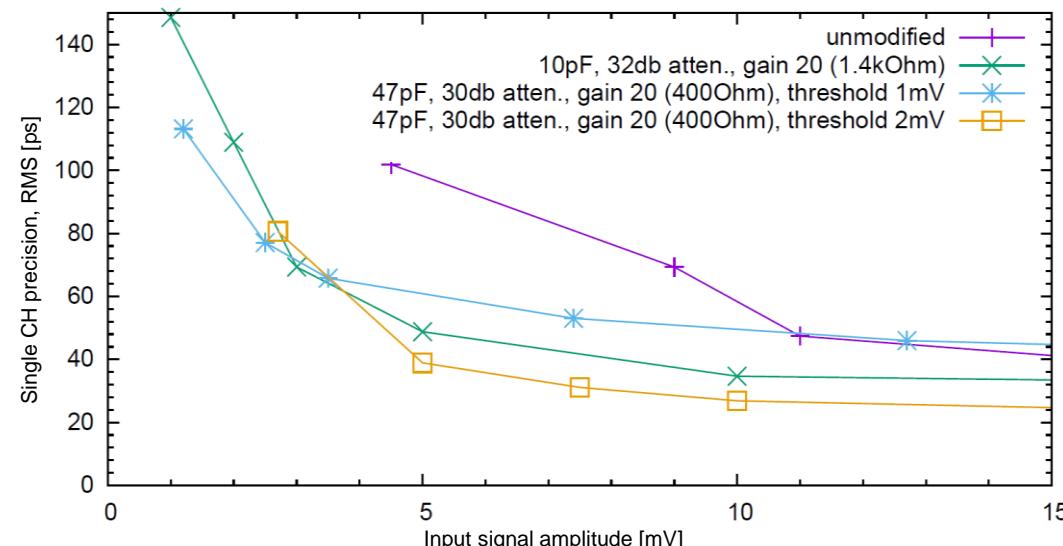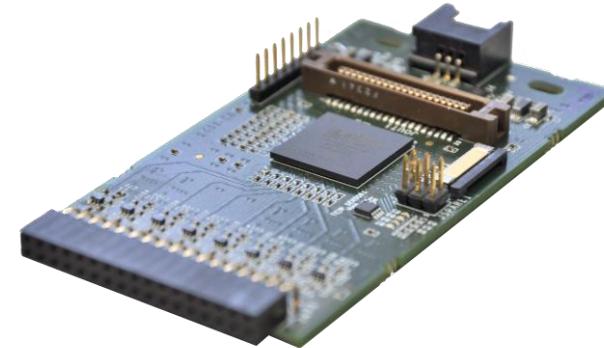
- 16 CH
- Amplification: 20-30 (depending on amplitude)
- Timing precision: ~30ps RMS
- Dynamic range: ~250
- Up to 16 PADIWA per TRB



TRB-PADIWA timing performance

TDC Hardware – MBS DAQ System

- 2 Gb/s optical interface via PCIe card
 - Up to 4 optical readouts per PCIe card with 200 MB/s each
 - Slow control over same interface
- 19" crate system with up to 19 modules (smaller backplanes available)
- System is scalable and well extendable (VME readout included)
- Various front-end modules
 - 10 ps FPGA TDC System
 - 50/100 MHz 16 CH ADC modules (500 MHz planned)
 - 128 CH ~300 ps RMS TDC module coming soon

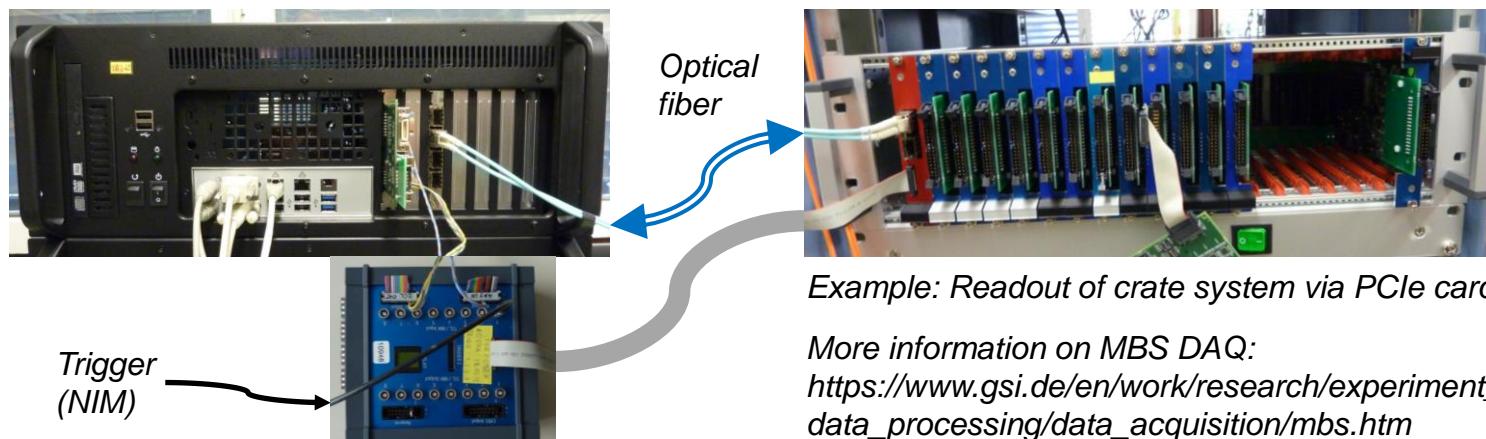

Example: Readout of crate system via PCIe card

More information on MBS DAQ:


https://www.gsi.de/en/work/research/experiment_electronics/data_processing/data_acquisition/mbs.htm

TDC Hardware – TAMEX Front-End

- TAMEX FPGA TDC system




TAMEX TDC module for 19" crate

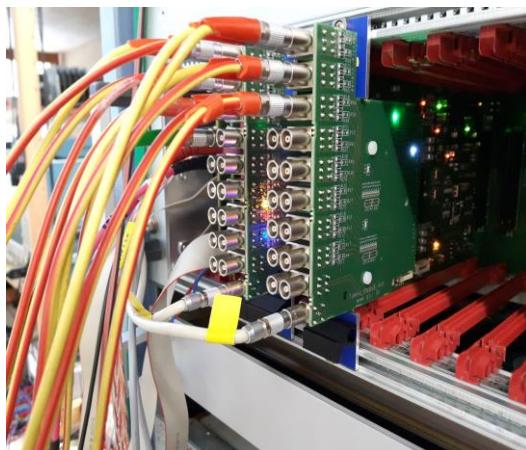

Modules with PADI discriminator front-ends in crate

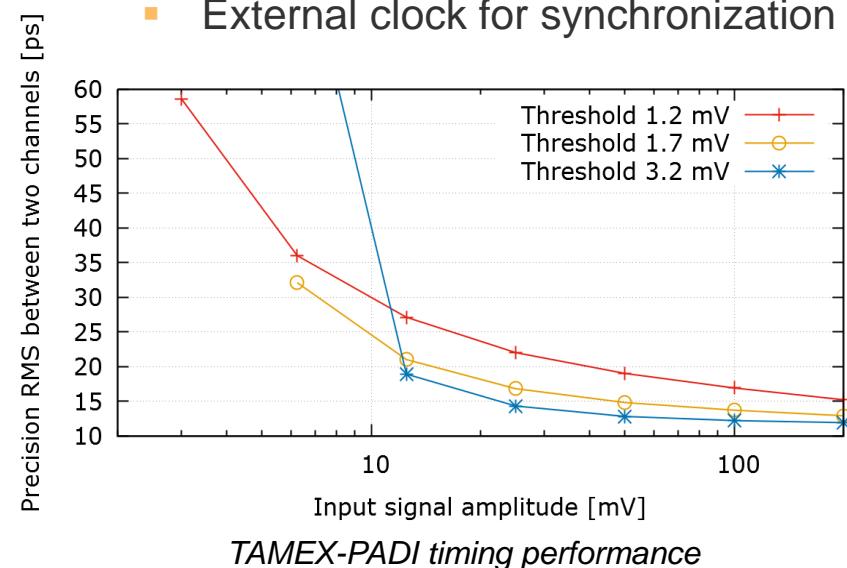- Up to 32 channels per FPGA / module (LVDS)
- Pre-amplifying & discriminating front-end with the PADI ASIC [4]
 - 16 CH leading & trailing edge
 - Channel dead time: $T_d = 20\text{ns}$
 - Amplification: ~ 200
 - Accepts signals down to few mV
 - External clock for synchronization



TDC Hardware – VME






VFTX – VME FPGA TDC X=10ps

- Inputs: LVDS, ECL, NIM
- Different TDC implementations available:
 - 16 CH, 7 ps RMS leading or trailing edge
 - 32 CH, 10 ps RMS leading or trailing edge
 - 16 CH, 10 ps RMS leading and trailing edge (ToT)
- Channel dead time:
 - 10 ps designs: $T_d = 40$ ns
 - 7 ps design: $T_d = 300$ ns
- Synchronization of multiple modules via external 200 MHz clock

GET4 TDC ASIC

GET4 – GSI Event driven TDC 4 CH

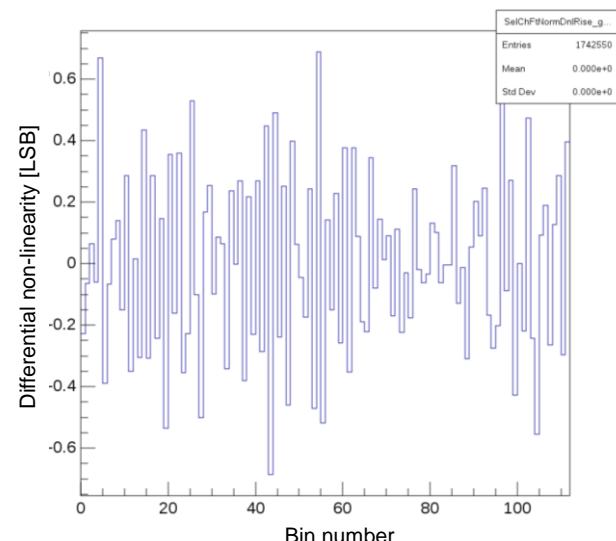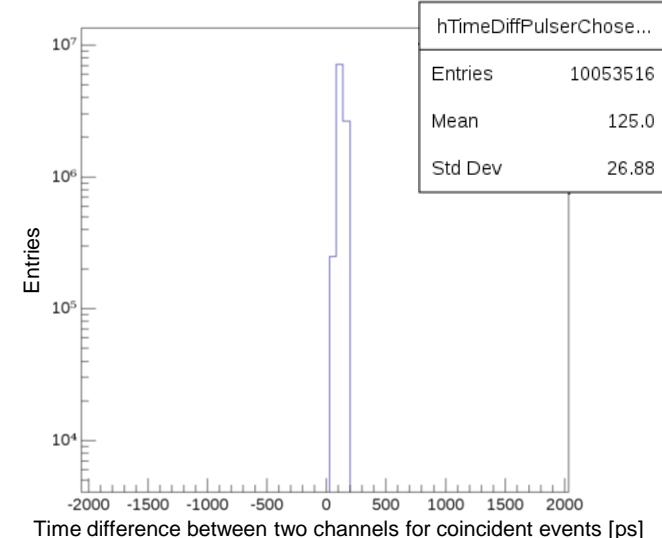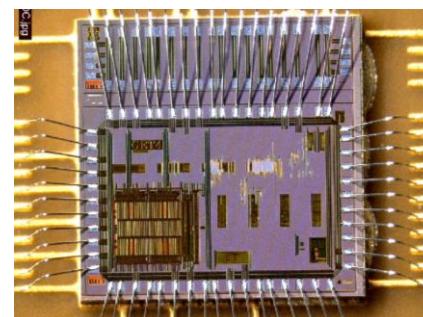- 4 CH LVDS in
- Delay line with 55 ps binning
- Diff. non-linearity: better than +/- 1 LSB
- Precision: ~26 ps (w/o calibration)
- Dead time: 3.2 ns
- Min. pulse width: 500 ps
- Leading edge & ToT measurement
- Free-streaming
- Radiation hardened



More information:

<https://wiki.gsi.de/pub/EE/GeT4/get4.pdf>

Questions?

Thank you for your attention!

Contacts:

General / TDC: Henning Heggen – h.heggen@gsi.de

TRB Platform: Michael Traxler – m.traxler@gsi.de

MBS DAQ System: Nikolaus Kurz – n.kurz@gsi.de



GET4 ASIC: Holger Flemming – h.flemming@gsi.de

References


- [1] C. Ugur *et al* 2016 *JINST* **11** C01046
A novel approach for pulse width measurements with a high precision (8 ps RMS) TDC in an FPGA
- [2] C. Ugur *et al* 2013 *IEEE Nordic Mediterranean Workshop on TDCs*
264 Channel TDC platform applying 65 channel high precision (7.2 ps RMS) FPGA based TDCs
- [3] J. Wu and Z. Shi 2008 *IEEE Nucl. Sci. Symp. Conf. Rec.* 3440
The 10-ps Wave Union TDC: Improving FPGA TDC Resolution beyond Its Cell Delay
- [4] M. Ciobanu *et al* 2014 *IEEE Transactions on Nucl. Sci.* **61** No. 2 105
PADI, an Ultrafast Preamplifier - Discriminator ASIC for Time-of-Flight Measurements

Stretcher & Single CH ToT Measurement

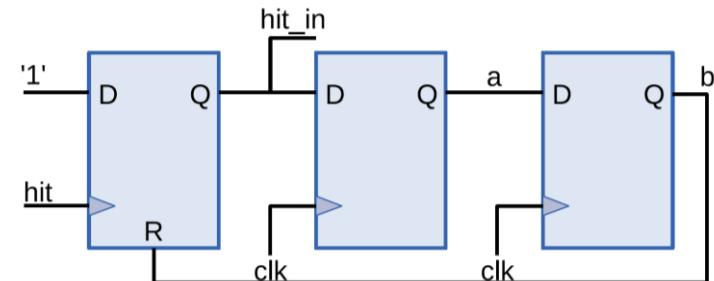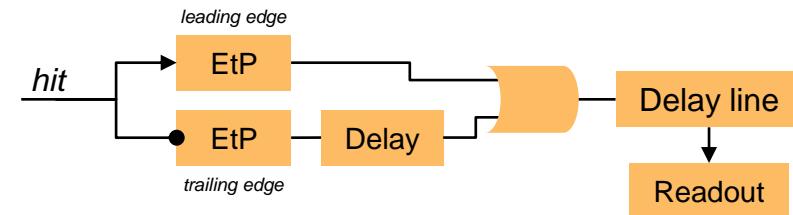- Delay line requires input signals wider than one clock period
- Semi-asynchronous edge-to-pulse (EtP) stage at every input
- Delay circuit allows serial measurement of both edges of a pulse in same CH
 - More channels but longer dead time: 30ns → 70ns




Semi-asynchronous pulse stretcher [1]

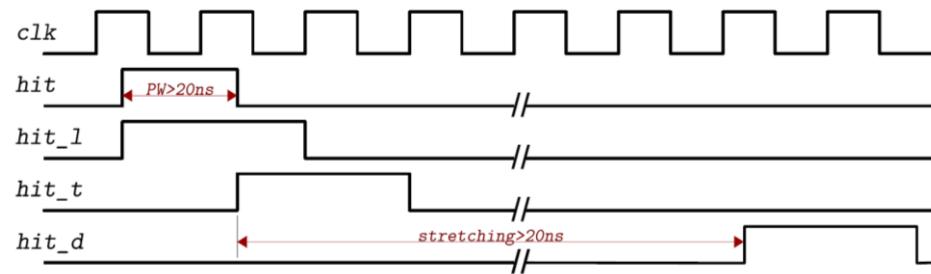

Timing diagram of the ToT measurement with stretcher [1]


FPGA TDC Potential

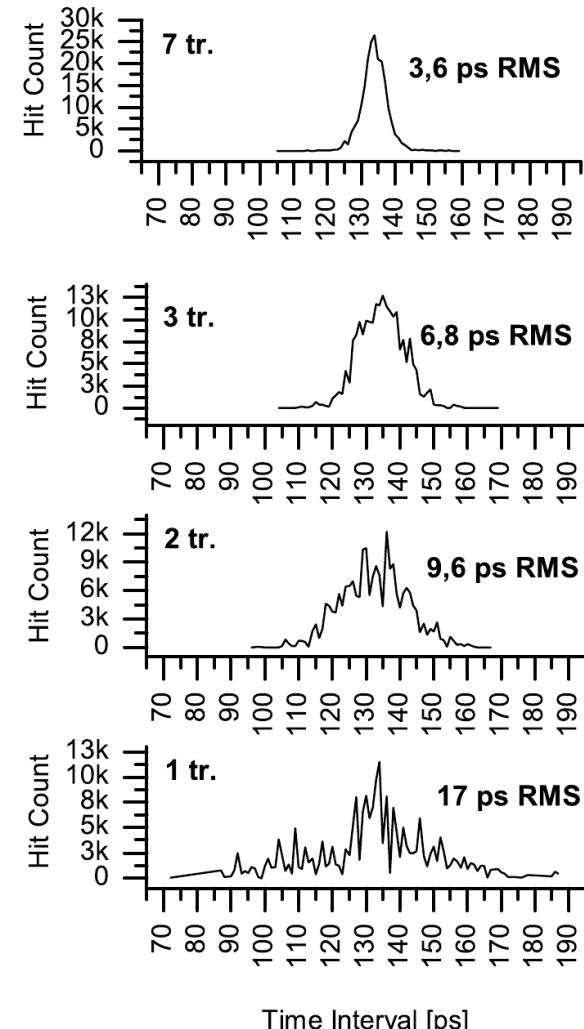- FPGA TDCs can be very precise
- But everything comes at a price
- Trade-off:
 - Precision
 - Number of CH (FPGA resources)
 - Channel dead time
(conversion time)




*Measured precision for different
TDC implementations on VIRTEX4 FPGA*

FPGA TDC Non-Linearity

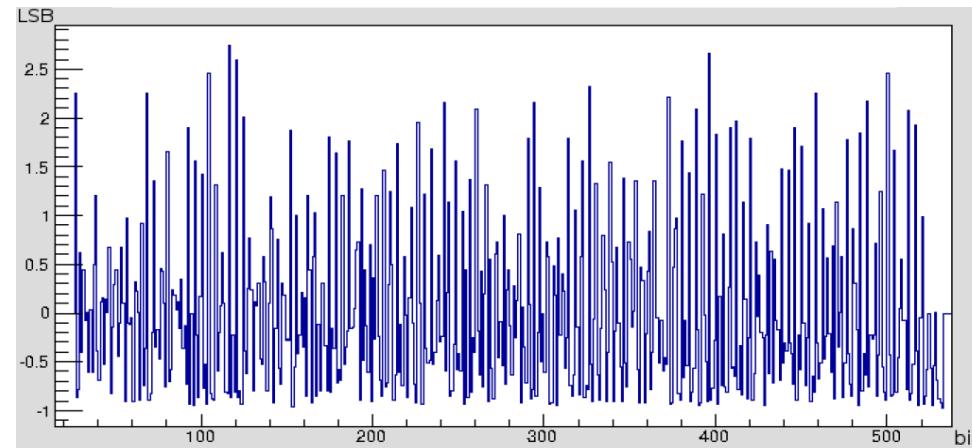


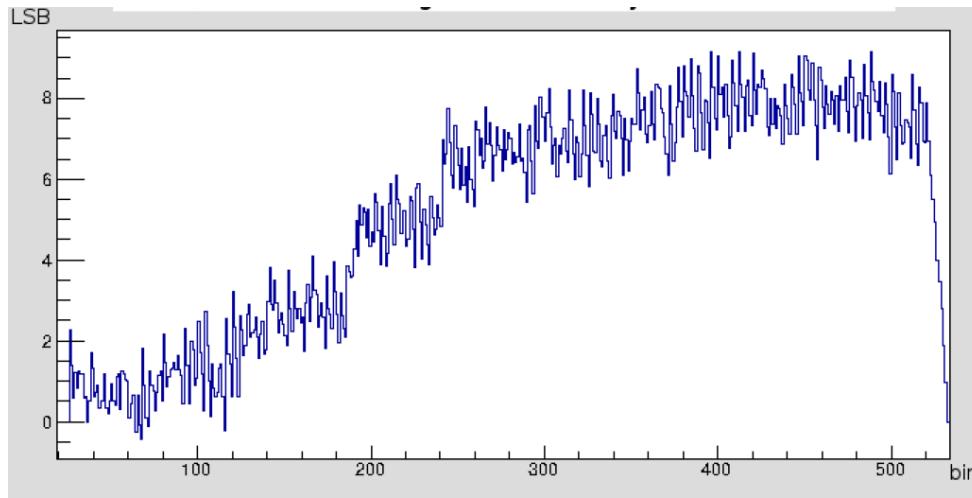Differential non-linearity of the FPGA TDC [2]




Integral non-linearity of the FPGA TDC [2]

TDC – ASIC vs. FPGA-TDC

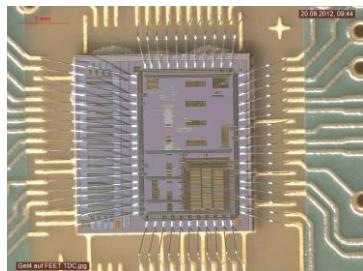

GET4 ASIC (GSI EE-ASIC)

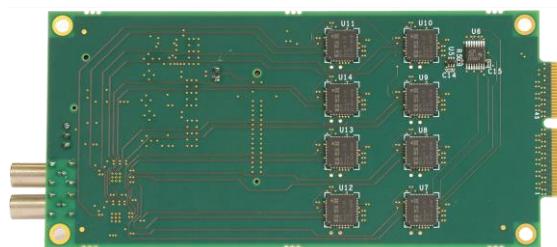

ASIC


- Radiation tolerance
- Power consumption
- Self-calibrated
- Dead time 3.2ns
- Price
- Availability can be an issue
- Flexibility



FPGA-TDC

- High precision
- Flexibility/ Firmware updates
- Availability
- Price
- Power consumption
- Calibration necessary
- Dead time 20ns (or higher)

TRB3

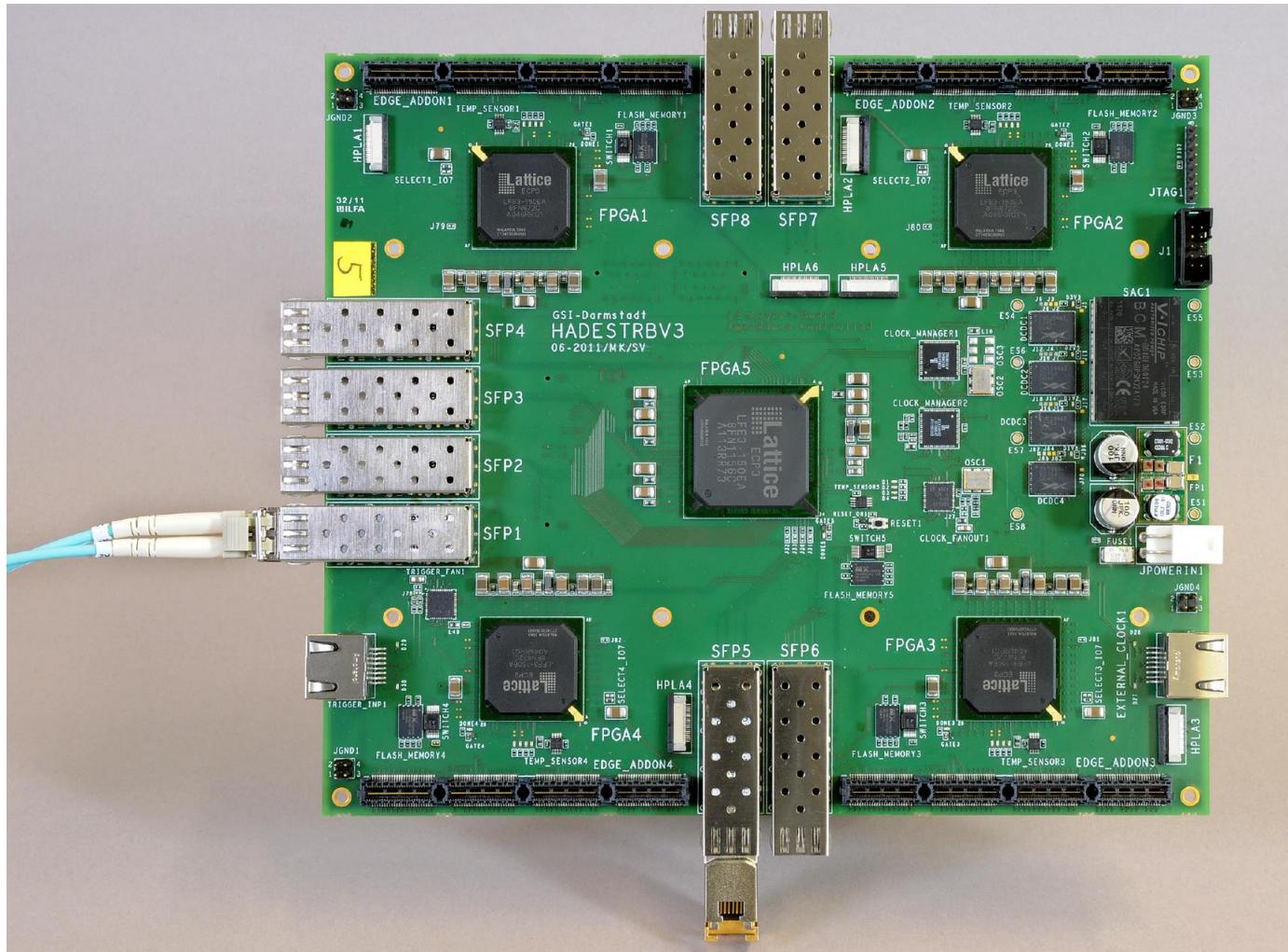


TDC Hardware – Front-Ends

PADIWA



Pre-amplifying & discriminating FEE

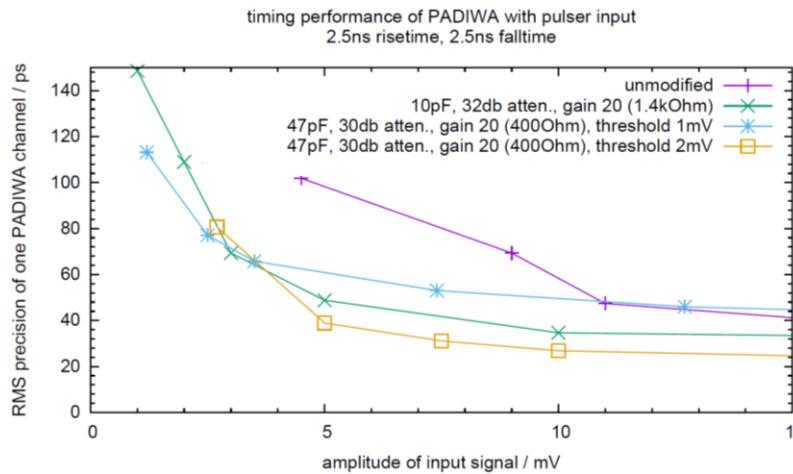
- 16 CH
- Timing precision: ~30ps RMS
- Amplification: 20-30 (depending on amplitude)
- Dynamic range: ~250



PADIWA-AMPS



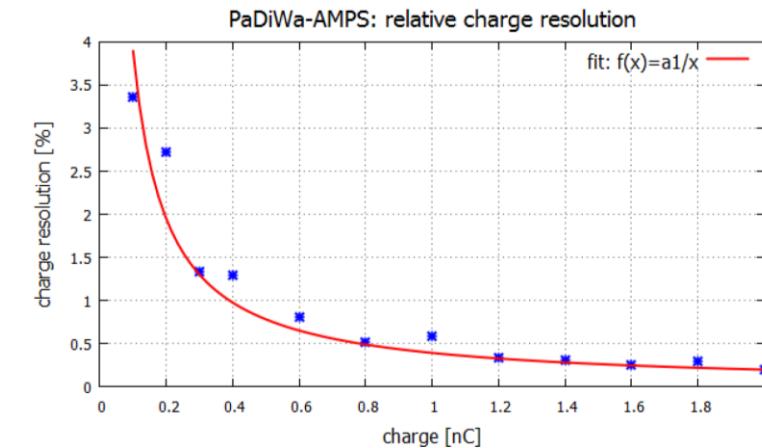
- PADIWA + Charge Integrator
- Charge measurement by ToT
- 8 CH
- Rel. charge resolution up to 0.5%




TDC Hardware – Front-Ends




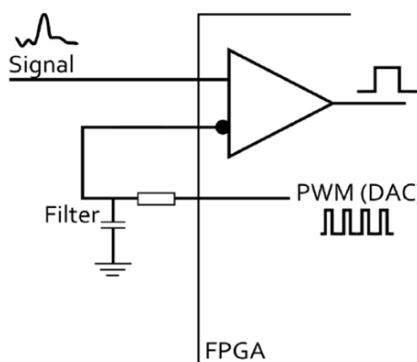
PADIWA
Pre-amplifying & discriminating FEE (16 CH)



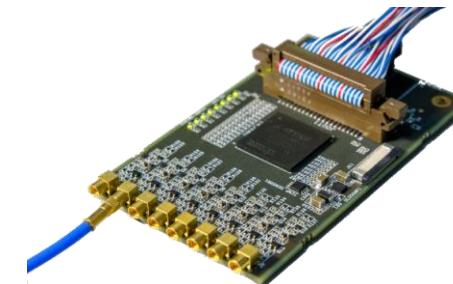- Timing precision: ~25ps
- Amplification: ~20-30 (depending on amplitude)
- Dynamic range: ~250



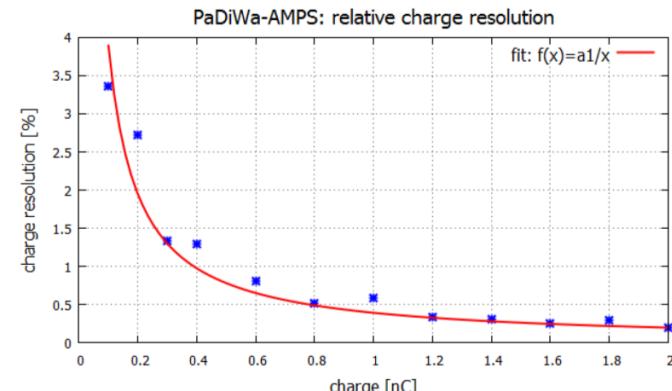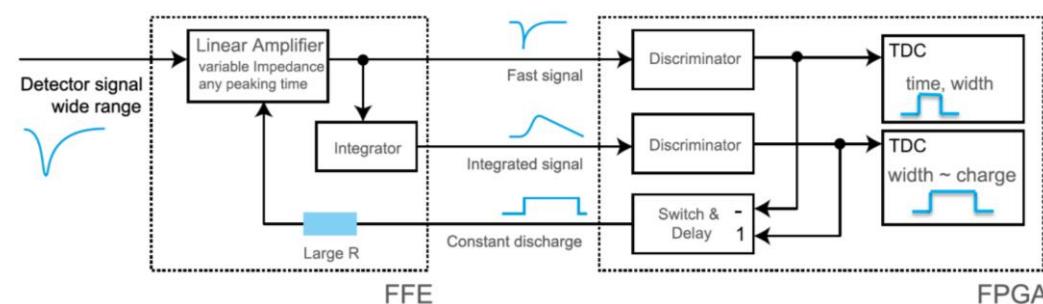PADIWA-AMPS
Charge-integrating FEE for charge measurements by ToT (8 CH)



Precision, Resolution, Accuracy?

